

# Lab 3

Ansel, Rowan


## Lab 3

3.1  
(a) Remeasured  $L_1$  from Lab 2:  $2.887 \pm 0.044 \text{ mH}$

$$\hookrightarrow \text{Predicted } L_2 = 4/25 = 115 \pm 1.8 \text{ mH}$$

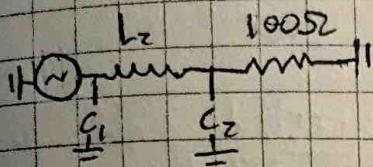(b) we want  $Z_r \sim Z_L$ , so if  $L_2 = 4/25 L_1$ ,  $Z_{L2} = 4/25 Z_{L1} \rightarrow R_2 \sim 1/25 R_1$

or  $4052 \rightarrow 100 \Omega$  for the resistance measurement



$$R_{\text{measured}} = 97.9 \pm 1.5 \Omega$$

$$L_{\text{measured}} = 108.2 \pm 11.6 \text{ mH}$$


(c) the half-turns on both the "25-turn" and "5-turn" inductors mess things up - after recalculating,  $(25.75/5.0)^2 \rightarrow$  predicted  $108.8 \pm 1.7 \text{ mH} \rightarrow$  agrees!

$$L_2 = 108 \text{ mH}$$

$$Z_L = i\omega L, \quad \omega = 2\pi \cdot 10^5$$

$$\hookrightarrow Z_1 = 1.148 \pm 0.019 \Omega, Z_2 = 65.62 \pm 1.7 \Omega$$

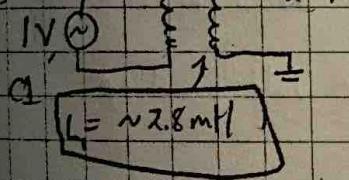$Z_1 \gg 22.5 \Omega$ , so it won't affect much



$$(b) V_{in} = 0.697 \text{ V}, V_{out} = 3.465 \pm 5 \text{ mV}, \frac{V_{out}}{V_{in}} = 4.97 \pm 0.04$$

agrees with 5.0!

$$T_{L2/L1} =$$

also agrees with  $N_{12} = 5.01 \pm 0.07$

$$(c) V_{in} = 1.0 \pm 0.005, V_{out} = 0.20 \pm 0.005 \rightarrow \frac{V_{out}}{V_{in}} = 0.198 \pm 0.005$$

agrees with 0.2!

and with  $N_{12} = 0.1995 \pm 0.0028$

$$(d) N_{12} = (L_1/L_2)^{1/2} = 3.01 \pm 0.07, k = \frac{V_{in}}{V_{out}} / N_{12} = 0.992 \pm 0.024$$

Pre-lab 3	5.01
3.2	✓
3.3	✓

(e)  $R = 21.7 \pm 0.2\Omega$ ,  $\Delta V_1 = 14.5 \pm 0.05 \text{ mV} \rightarrow I = 0.65 \pm 0.08 \text{ mA}$   
 no one could figure  $V_{\text{primary}} = 1.01 \pm 0.005 \text{ V} \rightarrow$   
 this out

$$Z_{\text{primary}} = V_{\text{primary}} / I = [1970 \pm 190.5] \Omega, \text{ does not agree w/ } 1648 \pm 14.5 \Omega$$

$$(f) R_L \approx R_p \cdot \frac{N_2}{N_1} \cdot \left( \frac{1}{R_p} \right)^2 = [8.24 \pm 0.32] \Omega$$

↳ geometric mean to be as far as possible

$$(g) V_1 = 111 \text{ mV}, V_2 = 0.632 \text{ V} \rightarrow \frac{V_1}{V_2} = 0.175, \text{ does not agree w/ } 0.2, 12\% \text{ discrepancy}$$

$$(h) I = \frac{0.117 \text{ A}}{22.2} = 5.08 \text{ mA} \rightarrow Z_p = \frac{V_2}{I} = \frac{0.632}{5.08 \times 10^{-3}} = [124.3] \Omega \text{ agrees w/ } 117 \Omega$$

it is lower than expectation, and it differs because

now that  $R_L \neq \infty$ , the 5-turn inductor can have much more current, and more energy can be transferred,

so the 25-turn inductor has a lower voltage drop  
 for equal current  $\rightarrow$  lower impedance

(i)

With  $4.7 \Omega$ : nearly in phase, slight lag in the resistor

with  $R_L = \infty \Omega$ : resistor lags behind inductor by about  $90^\circ$

with  $0.53 \mu\text{F}$ : there was a  $\sim 85^\circ$  trail in the resistor

when the load resistance increases,  $Z_L$  increases, which causes the circuit to act like a simple RL circuit, which is past its cutoff point.

when putting in a capacitor, the load becomes an LC circuit and the primary will transfer power based on the load cutoff points, meaning the phase will be impacted as with an RC circuit

(j)  $V = 0.11060 \text{ V}$ ,  $R = 1.75 \Omega \rightarrow I = V/R = [23.53 \text{ mA}]$

Compared to  $I_{\text{in}} = 5.08 \text{ mA}$ ,  $I_{\text{out}}/I_{\text{in}} = 4.63$ , does not agree with expectation of 5.01, 7% discrepancy.

3.3

(a)  $R = 9.98 \pm 0.10 \text{ k}\Omega$ ,  $C = 99.7 \pm 4 \text{ nF}$ ,  $L = 2.588 \pm 0.094$   
(remesured)

$$R_{\text{avg}} = \\ 222 \pm 27 \text{ k}\Omega$$

$$\omega_0 = (LC)^{-1/2} = (6.23 \pm 0.18) \cdot 10^4 \text{ rad/s} \rightarrow f_c = 9.91 \pm 0.29 \text{ kHz}$$

(b)  $f_{\text{measured}} = [10.359 \pm 0.090 \text{ kHz}]$ , does not agree with predicted - perhaps  $10 \text{ k}\Omega < 220 \text{ k}\Omega$ ?

(c)

$$-3 \pm 0.01 \text{ dB @ } \Delta x = +158.323 \text{ Hz} \rightarrow Q = \frac{10.359}{(0.158 \pm 0.144)} = [34.23 \pm 0.32]$$

$$-3 \pm 0.02 \text{ dB @ } \Delta x = -144.323 \text{ Hz}$$

(d)

<u>R</u>	<u><math>f_{\text{max}}</math></u>	<u>3dB pos</u>	<u>3dB neg</u>	<u>Q</u>
$989 \pm 10 \Omega$	$10.415 \text{ kHz}$	$+962 \pm 90 \text{ Hz}$	$-864 \pm 90 \text{ Hz}$	$5.7 \pm 0.4$
$2.93 \pm 0.034 \text{ k}\Omega$	$10.401 \text{ kHz}$	$+336 \pm 5 \text{ Hz}$	$-347 \pm 10 \text{ Hz}$	$15.23 \pm 0.26$

<u>R</u>	<u>Real</u>	<u>Agree?</u>
$10 \text{ k}$ : $Q = 6.9 \pm 1.9$	$34.23 \pm 0.32$	X
$3 \text{ k}$ : $Q = 18.2 \pm 0.6$	$15.23 \pm 0.26$	X
$1 \text{ k}$ : $Q = 6.14 \pm 0.19$	$5.7 \pm 0.4$	✓

(f) measured peak:  $271 \pm 5 \text{ mV} = V_C$

$$V_R = 4.868 \pm 0.0005 \text{ V} \rightarrow I = V_R / 222 \text{ k}\Omega = [0.0219 \pm 0.03 \text{ mA}]$$

~~$$I = I_o + I_L = V \left( \frac{1}{R_o} + \frac{1}{R_L} \right) \rightarrow R_C = \frac{V}{I} \left( \frac{1}{R_L} \right) = \frac{V R_L}{(I R_L - V)}$$~~

$$R_L \ll R_C \text{ at } \omega_0 \rightarrow R_C = V_C / I = [12.36 \pm 0.3 \text{ k}\Omega]$$

(g)

$$\omega_0 = 10294 \pm 0.05 \text{ kHz}, \omega_W = 106 \pm 1.3 \text{ kHz}, \omega_{Wz} = -34.8 \pm 2.5 \text{ kHz}$$


$\hookrightarrow Q = 72.7 \pm 1.5$ ; ideal =  $76.2 \pm 2.6$ , almost agreed!

(h)


	$Q_{\text{ideal}}$	measured	agreed?
$10k\Omega$ :	$34.0 \pm 0.9$	$34.23 \pm 0.32$	✓
$3k\Omega$ :	$14.6 \pm 0.4$	$15.23 \pm 0.26$	✗ (almost!)
$1k\Omega$ :	$5.65 \pm 0.14$	$5.7 \pm 0.4$	✓

## 3.1

The circuit:



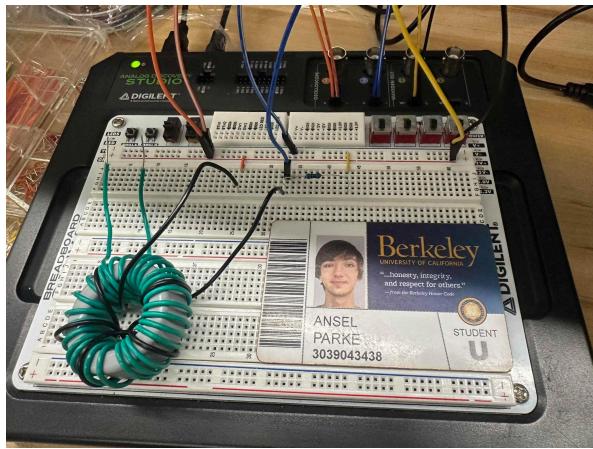


The inductance meter:


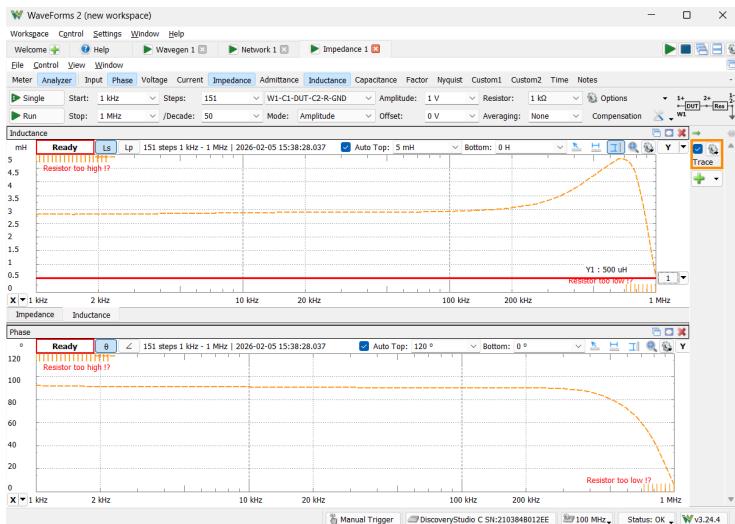


## 3.2

Step up and step down:

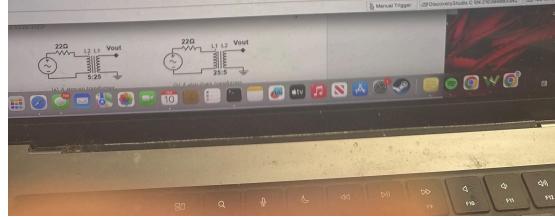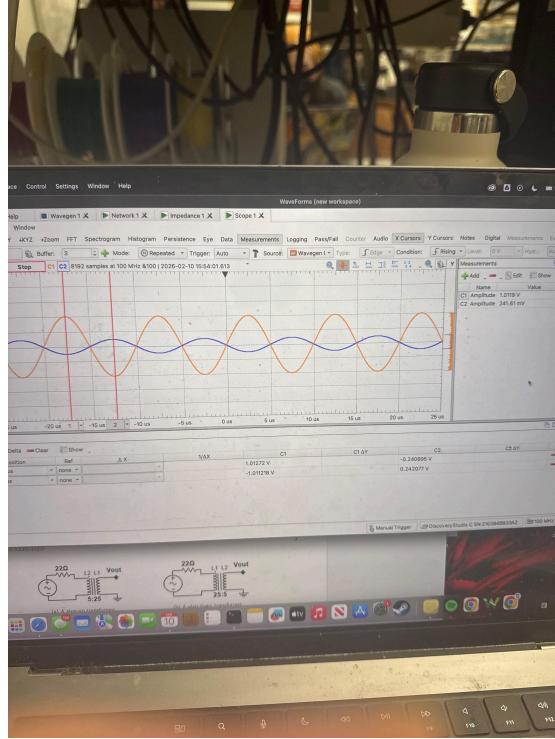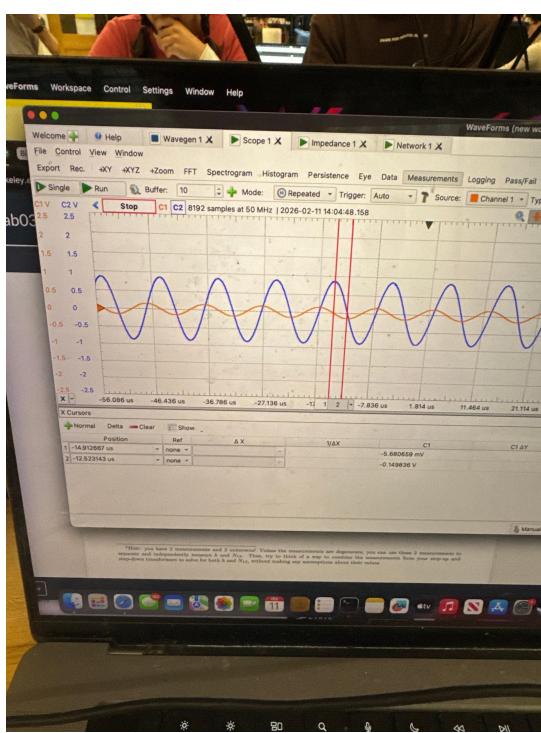

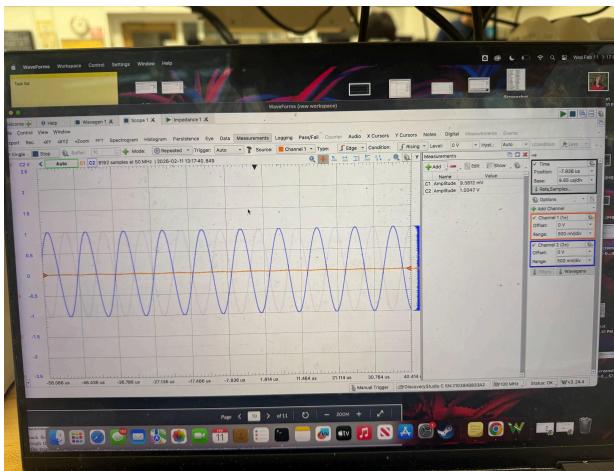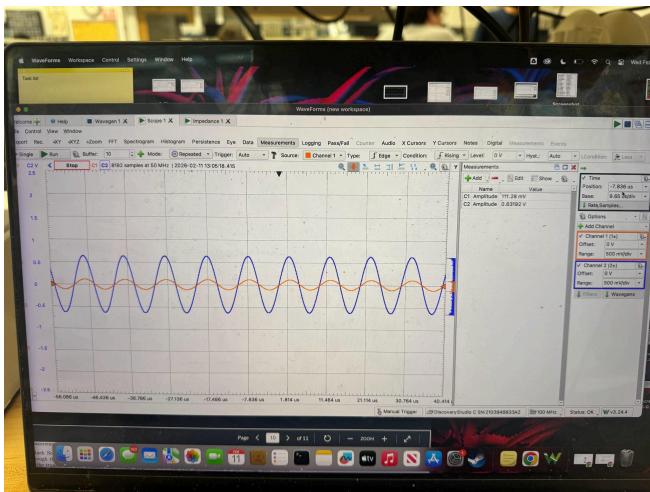
#### 4.7Ω resistor (without and then with)




### 3.3


The circuit:

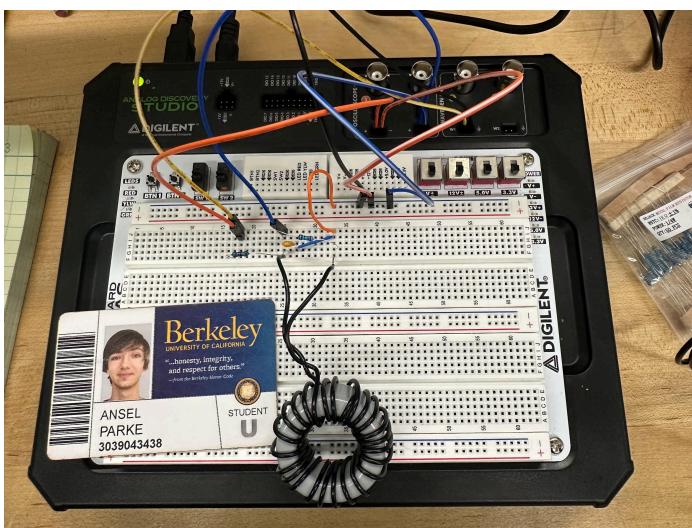


### 10kΩ network analyzer:

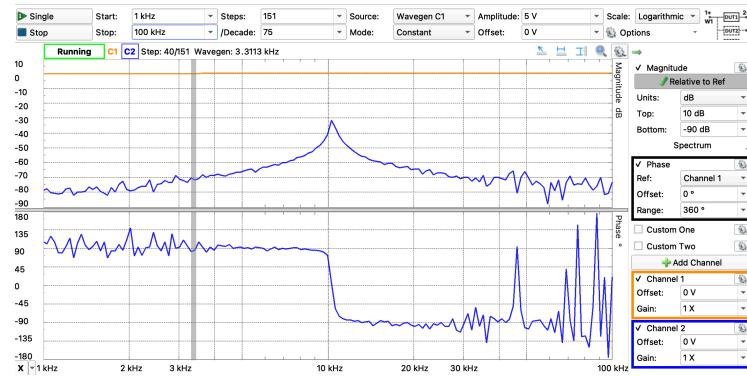

### 3kΩ network analyzer:

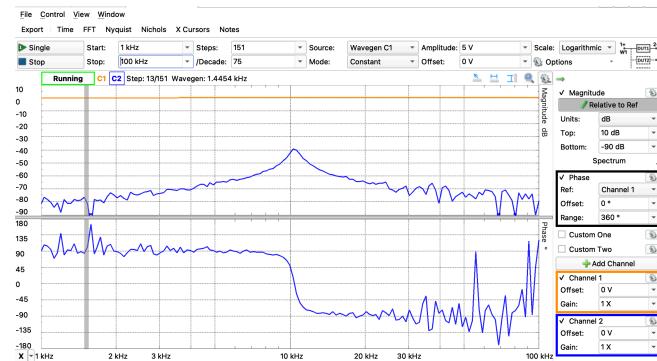

### 1kΩ network analyzer:

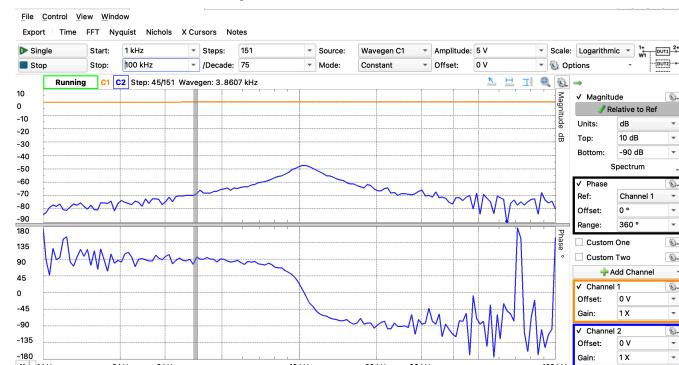

### 0kΩ network analyzer:

