

Lab 1

Physics 11A Spring 2026, Jan. 29

Ansel Parke, Smridhi Mahajan

1.1

(a)

Resistor

1

2

3

4

5

Resistance $\pm 0.15 \text{ k}\Omega$ (1%) ^{from data sheet}9.90 \rightarrow 9.909.89 \rightarrow 9.90 repeat

9.97

9.95

9.93

all agree w/ $10 \text{ k}\Omega \pm 0.1 \text{ k}\Omega$

manufacturer spec

(b)

Capacitor

1

2

3

4

5

Capacitance

 $9.39 \pm 0.43 \text{ nF}$ $9.90 \pm 0.45 \text{ nF}$ $9.66 \pm 0.44 \text{ nF}$ $8.57 \pm 0.39 \rightarrow$ does not agree w/ $10 \pm 1 \text{ nF}$ $9.28 \pm 0.47 \text{ nF}$

1.2

Voltage Source



 $\pm 12\text{V}$ -12V $\pm 5\text{V}$ $\pm 3.3\text{V}$

Voltage

 $12.09 \pm 0.17 \text{ V}$ $-12.10 \pm 0.17 \text{ V}$ $5.06 \pm 0.1 \text{ V}$ $3.31 \pm 0.08 \text{ V}$

all agree!

1.3

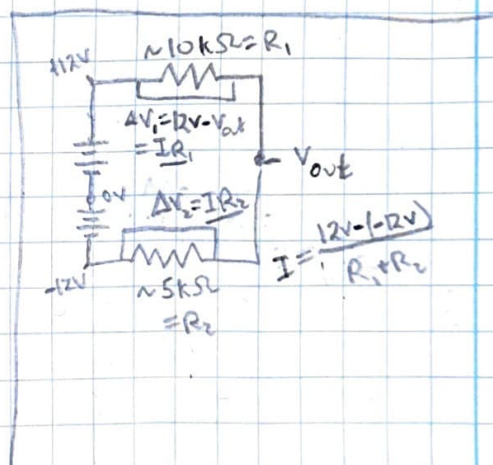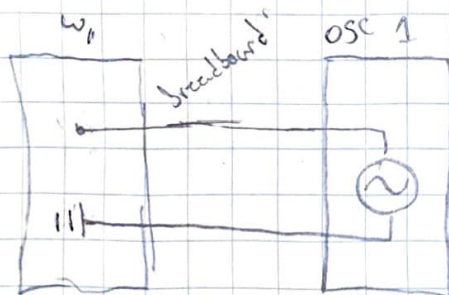

1.4

(a) total $V: 24\text{V}$, total $R: 15.1 \text{ k}\Omega \rightarrow \Delta V_1 = R_1 I, \Delta V_2 = R_2 I$ \rightarrow total $I = 1.59 \text{ mA}$ $\Delta V_1 = 15.9 \text{ V}, \Delta V_2 = 8.1 \text{ V}$ $V_{out} = 12\text{V} - \Delta V_1 = -3.9 \text{ V} = V_{out}$ (b) $R_1 = 9.90 \pm 0.15 \text{ k}\Omega, R_2 = 5.01 \pm 0.1 \text{ k}\Omega$ $I = 1.622 \pm 0.250 \text{ mA}, V_1 = 16.66 \pm 0.21 \text{ V}, V_2 = 8.128 \pm 0.158 \text{ V}$ $V_{out} = -3.97 \pm 0.27 \text{ V}$


w/ margin of error, mostly

1.4

(C) measured $V_{out} = -3.97 \pm 0.087$ V relative to ground(d) measured $\Delta V_1 = 16.05 \pm 0.21$ V, $\Delta V_2 = 8.13 \pm 0.13$ V(e) measured $I = 1.602 \pm 0.032$ mA(f) calculated $R_1 = 9.900 \pm 0.150$ k Ω
 $R_2 = 5.01 \pm 0.10$ k Ω L2.11
1/26/26

1.5

Re-drawing the circuit here:

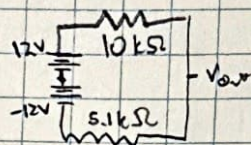

(a) $P = (\Delta V)^2 / R$

$$L_1 P_1 = (15.89)^2 / 10k = 0.0253 \text{ W}$$

$$L_2 P_2 = (8.11)^2 / 5.1k = 0.0129 \text{ W}$$

↓

(b) $R_{min} = (24V)^2 / 0.25W = 2304 \Omega$

(c) R_1/R_2 is the same $\rightarrow V_1, V_2$ are the same

$$\text{for } V_1: R_{1,min} = (15.89)^2 / 0.25 = 1010 \Omega \approx 0.1 R_1$$

$$\text{for } V_2: R_{2,min} = (8.11)^2 / 0.25 = 262 \Omega \approx 0.05 R_2$$

Resistor 1 hits 0.25W first (scaling geometrically) at 1010Ω

$$(d) \left(\frac{1010}{10000} \right) (5100 \Omega) = 515 \Omega \rightarrow P_2 = (8.11)^2 / 515 = 0.128 \text{ W}$$

$$\rightarrow P_{total} = 0.25W + 0.128W = 0.378 \text{ W}$$

1.6

$$(a) \int_0^{2\pi/\omega} \sin^2(\omega t) dt = \frac{1}{2}x - \frac{1}{4\omega} \sin(2\omega x) \Big|_0^{2\pi/\omega} = \frac{\pi}{\omega} \rightarrow \langle \sin^2(x) \rangle = \frac{\omega}{2\pi} \left(\frac{\pi}{\omega} \right) = \frac{1}{2}$$

$$\rightarrow \boxed{V_{RMS} = 2^{-1/2}} \cdot \text{Amplitude}$$

$$(b) f(x) = \begin{cases} 1-x & x \in (0,2) \\ -3+x & x \in (2,4) \end{cases} \rightarrow (f(x))^2 = \begin{cases} (x-1)^2 & 0 \leq x \leq 2 \\ (x-3)^2 & 2 \leq x \leq 4 \end{cases} \rightarrow$$

$$\int_0^4 f(x) = \frac{(x-1)^3}{3} \Big|_0^2 + \frac{(x-3)^3}{3} \Big|_2^4 = \frac{1}{3}(4) \rightarrow V_{RMS} = \left(\frac{4}{3} \right)^{1/2} = \boxed{3^{-1/2}} \cdot \text{Amplitude}$$

$$(c) |\text{square wave}| = 1 \rightarrow \text{average} = 1 \rightarrow \boxed{V_{RMS} = 1} \cdot \text{Amplitude}$$

1.7

$$(a) 0.708 \pm 0.017 \text{ V (From DMM)}$$

$$(b) 707.1 \pm 0.05 \text{ mV (From ADS Voltmeter)}$$

$$(c) 0.69858 \pm 0.000005 \text{ V (From ADS Scope)}$$

↳ this value agrees with the DMM measurement!


$$(d) \text{Peak2Peak: } 2.0021 \text{ V} \pm 5e-5 \text{ V}$$

$$\text{Amplitude: } 0.99405 \text{ V} \pm 5e-6 \text{ V}$$

$(\times 2^{-16})$ ↳ expected $V_{RMS}: 0.70643 \pm 4e-6 \rightarrow$ does not agree w/ ADS, but does agree with DMM - errors were underestimated

(e)	Frequency / V_{RMS} with: DMM ^(N)	ADS Voltmeter (mV)	ADS Measurements (V)	
	10	0.667 \pm 0.017	707.3 \pm 0.05	0.70706 \pm 5e-6
	20	0.698 \pm 0.017	707.3 \pm 0.05	0.70695 \pm 5e-6
	50	0.707 \pm 0.017	707.2 \pm 0.05	0.70704 \pm 5e-6
	100	0.708 \pm 0.017	707.1 \pm 0.05	0.70696 \pm 5e-6
	200	0.709 \pm 0.017	707.1 \pm 0.05	0.70696 \pm 5e-6
	500	0.708 \pm 0.017	703.2 \pm 0.05	0.70694 \pm 5e-6
	1000	0.705 \pm 0.017	694.1 \pm 0.05	0.70695 \pm 5e-6
	2000	0.682 \pm 0.017	643.1 \pm 0.05	0.70705 \pm 5e-6
	5000	0.352 \pm 0.013	352.9 \pm 0.05	0.70733 \pm 5e-6
	10000	0.039 \pm 0.009	120.5 \pm 0.05	0.70552 \pm 5e-6

1.8

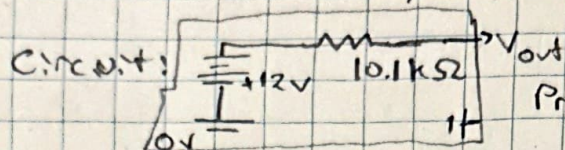(a) Measured: 6.02 ± 0.09 V, 0.594 ± 0.017 mA $\rightarrow 10.1 \pm 0.3$ k Ω 

Predicted: $5.1k + \left(\frac{1}{10k} + \frac{1}{10k}\right)^{-1}$
 $= 5.1k + \frac{10k}{2} = 10.1k\Omega$ ✓

(b)


R_L	V_{out} (V)	I_{out} (mA)
330 Ω	0.193 ± 0.01	0.58 ± 0.01
1k Ω	0.538 ± 0.015	0.54 ± 0.01
3k Ω	1.364 ± 0.026	0.45 ± 0.01
10k Ω	3.00 ± 0.05	0.3 ± 0.01
33k Ω	4.60 ± 0.07	0.14 ± 0.003
100k Ω	5.46 ± 0.08	0.055 ± 0.001

Full plot in pdf

all values agreed!

measured resistance = 9.94 ± 0.10 k Ω it agrees but only w/ 0.5 \rightarrow with theory

1.9

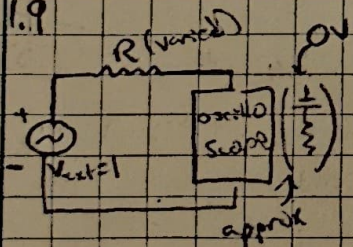

$$I = \frac{V_{ext}}{R + Z_{th}}$$

R	measured V_{in}
0 Ω	$0.999 \pm 5e-4$
100k Ω	$0.91 \pm 5e-3$
1M Ω	$0.51 \pm 5e-3$
5.6M Ω	$0.1 \pm 5e-2$

$$V_{in}(R + Z_{th}) = V_{ext}(Z_{th})$$

$$\rightarrow Z_{th} = R(V_{in}/(V_{ext} - V_{in}))$$

Predicted Z_{th}

$$0 \pm \infty \Omega \rightarrow \text{discarded}$$

$$\rightarrow 1.01 \pm 0.07 \text{ M}\Omega$$


$$1.041 \pm 0.033 \text{ M}\Omega$$

$$1.0 \pm 0.4 \text{ M}\Omega$$

$$\rightarrow \text{Avg: } 1.01 \pm 0.13 \text{ M}\Omega$$

1.10

(a)

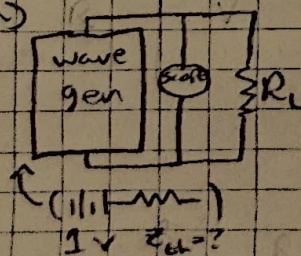

$$R_L = \infty$$

$$V_s = 1V$$

$$(0.999 \pm 5e-4)$$

(b) $R(\Omega)$ $V(V)$ $Z_{wavegen}$


33	$0.39 \pm 5e-3$	$54.6 \pm 1.6 \Omega$
100	$0.66 \pm 5e-3$	$\rightarrow 51.5 \pm 1.7 \Omega$
330	$0.86 \pm 5e-3$	$53.7 \pm 2.5 \Omega$
1k	$0.93 \pm 5e-3$	$53 \pm 6 \Omega$

$$V_{out} = V_{th} \left(\frac{R}{R + Z_{th}} \right) \rightarrow Z_{th} = R \left(\frac{1}{V_{out}} - 1 \right)$$

$$R = (R_{source} + R_L) \approx R_L$$

$$\text{Final: } 52.4 \pm 1.7 \Omega$$

1.11

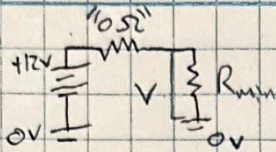

$$P = V^2/R = 0.25 \text{ W} \rightarrow R_{\min} = \frac{12^2}{0.25} = 576 \Omega$$

DMM measured $11.93 \pm 0.12 \text{ V}$ with $680 \Omega \pm 7$


Load circuit?

vs $12.09 \pm 0.17 \text{ V}$ from earlier

$$(12.09) \frac{R_{\min}}{R_{\min} + Z} = 11.93 \rightarrow Z_{\min} = R_{\min} \left(\frac{12.09}{11.93} - 1 \right) = 680 \left(\frac{12.09}{11.93} - 1 \right) = 9 \pm 14 \Omega$$

12

for voltage:

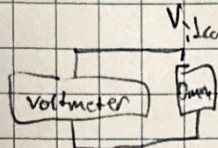Setting open voltage R_L

VS 01/2R

load voltage

Setting	open voltage	R_L	load voltage
200	$1.04 \pm 5e-3$	100	$0.990 \pm 5e-4$
2k	$1.04 \pm 5e-3$	1k	$0.266 \pm 5e-4$
20k	$1.08 \pm 5e-3$	10k	$0.473 \pm 5e-4$
200k	$1.03 \pm 5e-3$	100k	$0.504 \pm 5e-4$
2M	$0.709 \pm 5e-4$	1M	$0.415 \pm 5e-4$

 $V_D = V_{Th}$ $Z_v \approx 1 \text{ M}\Omega, V_v = 0$ $\sim V_{Th}$? only if $R_{\text{voltmeter}} \gg R_{DMM} = R_D \approx R_{Th}$

$$V_D = V_D \left(\frac{Z_v}{Z_v + R_D} \right) \approx V_D, R_D = (Z_v^{-1} + R_L^{-1})^{-1}, V_L = V_D \left(\frac{R_D}{R_D + R_D} \right) \rightarrow$$


$$R_D = R_L \left(\frac{V_D}{V_L} - 1 \right)$$

$$V_D \left(\frac{Z_v + R_D}{Z_v} \right) = V_L \left(\frac{R_D + R_D}{R_D} \right)$$

$$\rightarrow R_D = \frac{(R_L V_D Z_v - R_L V_L Z_v)}{(Z_v V_L - R_L V_D)} \rightarrow V_D = V_D \left(\frac{Z_v + R_D}{Z_v} \right)$$

calculations:

Setting	$R_L (\Omega)$	$R_D (\Omega)$	$V_D (V)$
200	~ 100	$10.1 \pm 0.8 e3$	$1.04 \pm 5e-3$
2k	$\sim 1k$	$3.1 \pm 0.09 e3$	$1.093 \pm 5e-3$
20k	$\sim 9.9k$	$1.300 \pm 0.034 e4$	$1.094 \pm 5e-3$
200k	$\sim 91k$	$1.16 \pm 0.04 e5$	1.148 ± 0.019
2M	$\sim 500k$	$2.4 \pm 0.8 e6$	2.4 ± 0.7

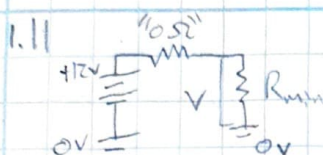


$$P = V^2/R = 0.25 \text{ W} \rightarrow R_{\min} = \frac{12^2}{0.25} = 576 \Omega$$

DMM measured $11.93 \pm 0.12 \Omega$ with $680 \Omega \pm 7$
 vs $12.09 \pm 0.17 \Omega$ from earlier

$$(12.09) \frac{R_{\min}}{R_{\min} + Z} = 11.93 \rightarrow Z_{\min} = R_{\min} \left(\frac{12.09}{11.93} - 1 \right) = 680 \left(\frac{12.09}{11.93} - 1 \right) = 9 \pm 14 \Omega$$

1.12

for voltage:

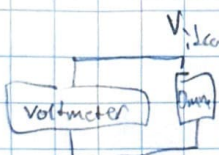

Setting open voltage R_L

VS 01/2R

load voltage

Setting	open voltage	R_L	load voltage
200	$1.04 \pm 5e-3$	100	$0.990 \pm 5e-4$
2k	$1.04 \pm 5e-3$	1k	$0.266 \pm 5e-4$
20k	$1.08 \pm 5e-3$	10k	$0.473 \pm 5e-4$
200k	$1.03 \pm 5e-3$	100k	$0.504 \pm 5e-4$
2M	$0.709 \pm 5e-4$	1M	$0.415 \pm 5e-4$

 $V_D = V_{Th}$

$$Z_v \approx 1 \text{ M}\Omega, V_v = 0$$

$\sim V_{Th}$? only if $R_{\text{voltmeter}} \gg R_{DMM} = R_D \equiv R_{Th}$

$$V_o = V_D \left(\frac{Z_v}{Z_v + R_D} \right) \approx V_D, R_c = (Z_v + R_L)^{-1}, V_L = V_D \left(\frac{R_c}{R_c + R_D} \right) \rightarrow$$

↓


$$R_D = R_c \left(\frac{V_D}{V_L} - 1 \right)$$

$$V_o \left(\frac{Z_v + R_D}{Z_v} \right) = V_L \left(\frac{R_c + R_D}{R_c} \right)$$

$$\rightarrow R_D = \frac{(R_c V_o Z_v - R_c V_L Z_v)}{(Z_v V_L - R_c V_o)} \rightarrow V_D = V_o \left(\frac{Z_v + R_D}{Z_v} \right)$$

calculations:

Setting	$R_c (\Omega)$	$R_D (\Omega)$	$V_D (V)$
200	~ 100	10.1 ± 0.8	$1.04 \pm 5e-3$
2k	$\sim 1k$	$3.11 \pm 0.09 e3$	$1.093 \pm 5e-3$
20k	$\sim 9.9k$	$1.300 \pm 0.034 e4$	$1.094 \pm 5e-3$
200k	$\sim 91k$	$1.16 \pm 0.04 e5$	1.148 ± 0.019
2M	$\sim 500k$	$2.4 \pm 0.8 e6$	2.4 ± 0.7

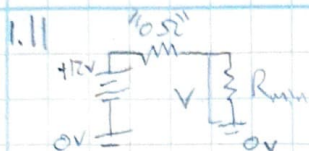

$$P = V^2/R = 0.25 \text{ W} \rightarrow R_{\min} = \frac{12^2}{0.25} = 576 \Omega$$

DMM measured $11.93 \pm 0.12 \text{ V}$ with $680 \Omega \pm 7$
vs $12.09 \pm 0.17 \text{ V}$ from earlier

$$(12.09) \frac{R_{\min}}{R_{\min} \pm 2} = 11.93 \rightarrow Z_{\min} = R_{\min} \left(\frac{12.09}{11.93} - 1 \right) = 680 \left(\frac{12.09}{11.93} - 1 \right) = 9 \pm 14 \Omega$$

1.12

for voltage:



Setting open voltage R_L load voltage

200	$1.09 \pm 5e-3$	100	$0.990 \pm 5e-4$
2k	$1.09 \pm 5e-3$	1k	$0.266 \pm 5e-4$
20k	$1.08 \pm 5e-3$	10k	$0.473 \pm 5e-4$
200k	$1.03 \pm 5e-3$	100k	$0.504 \pm 5e-4$
2M	$0.709 \pm 5e-4$	1M	$0.415 \pm 5e-4$

$V_D \equiv V_{Th}$

$$Z_v \approx 1 \text{ M}\Omega, V_v = 0$$

$\sim V_{Th}$? only if $R_{\text{voltmeter}} \gg R_{DMM} = R_D \equiv R_{Th}$

$$V_o = V_D \left(\frac{Z_v}{Z_v + R_D} \right) \approx V_D, R_c = (Z_v^{-1} + R_c^{-1})^{-1}, V_L = V_D \left(\frac{R_c}{R_c + R_D} \right) \rightarrow$$


$$R_D = R_c \left(\frac{V_D}{V_L} - 1 \right)$$

$$V_o \left(\frac{Z_v + R_D}{Z_v} \right) = V_L \left(\frac{R_c + R_D}{R_c} \right)$$


$$\rightarrow R_D = \frac{(R_c V_o Z_v - R_c V_L Z_v)}{(Z_v V_L - R_c V_o)} \rightarrow V_D = V_o \left(\frac{Z_v + R_D}{Z_v} \right)$$

calculations:

Setting	$R_c (\Omega)$	$R_D (\Omega)$	$V_D (V)$
200	~ 100	10.1 ± 0.8	$1.09 \pm 5e-3$
2k	$\sim 1k$	$3.11 \pm 0.09 e3$	$1.093 \pm 5e-3$
20k	$\sim 9.9k$	$1.300 \pm 0.034 e4$	$1.094 \pm 5e-3$
200k	$\sim 91k$	$1.16 \pm 0.04 e5$	1.148 ± 0.019
2M	$\sim 500k$	$2.4 \pm 0.8 e6$	2.4 ± 0.7

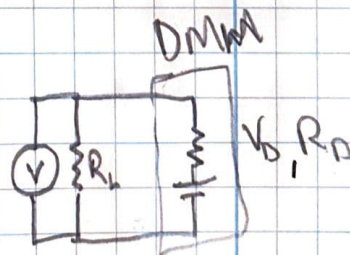

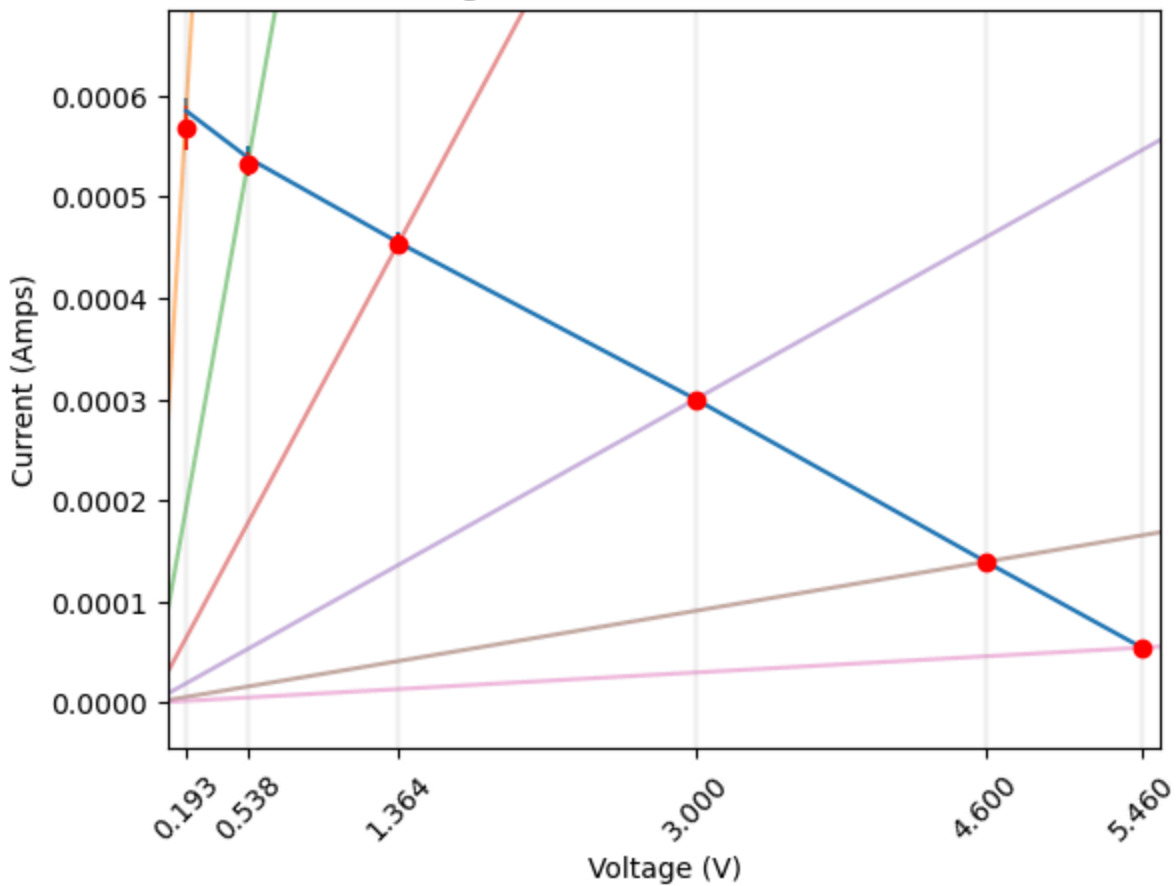Current Vs Voltage for different values of load resistance



- Thevenin prediction ($R_L=330$) for full voltage range
- Thevenin prediction ($R_L=1000$) for full voltage range
- Thevenin prediction ($R_L=3000$) for full voltage range
- Thevenin prediction ($R_L=10000$) for full voltage range
- Thevenin prediction ($R_L=33000$) for full voltage range
- Thevenin prediction ($R_L=100000$) for full voltage range
- + Inferred/Measured current/voltage values
- ◆ Thevenin prediction (only plotting the corresponding V_{out})